

MAHATMA GANDHI UNIVERSITY

M.C.A DEGREE EXAMINATION

MODEL QUESTION PAPER

(2011 Revised Syllabi)

First Semester

MCA 102 DIGITAL SYSTEMS AND LOGIC DESIGN

Time : Three hours

Maximum : 75 Marks

Part A

Answer any ten questions.

- 1 Perform following subtraction using 2's complement method.
(a) 01100-01001 (b) 0011.1001-0001.1110
- 2 Encode the following decimal numbers into excess 3 code.
(a) 327.89 (b) 20.305
- 3 Briefly describe the concept of hamming code.
- 4 Solve the following expressions using Boolean Algebraic theorem.
 $A' B C + A B' C + A B C' + A B C$
- 5 Why NAND gate is called as universal gate? Establish the statement.
- 6 Develop the logic circuit for a Full Adder.
- 7 Explain the working of RS flip flops.
- 8 Brief notes on serial in parallel out registers.
- 9 Draw the diagram of a 3 bit counter using Flip Flops.
- 10 Compare impact and Non impact printer.
- 11 What is sector interleave ?
- 12 Write a short note on the working of scanner.

(10 x 3 = 30 marks)

Part B

All questions carry equal marks.

- (a) Explain various binary codes used in digital system with the help of examples.

Or

- (b) Convert the decimal number 258.763 to (1) binary (2) octal (3) hexadecimal.
- 13 (a) Explain any three logic gates with truth table and logic diagram.

Or

- (b) Describe the minimization of Boolean function using K map method with suitable example.
- 14 (a) Explain the use of multiplexers and demultiplexers with logic diagram.

Or

- (b) With the aid of truth table and logic diagram, explain the working of a Master slave flip flop.
- 15 (a) Draw the logic diagram and timing characteristics of bidirectional shift registers.

Or

- (b) Draw the circuit and explain the working of an asynchronous decade Counter.
- 16 (a) Explain the different components of Hard disk.

Or

- (b) Explain the working of a Dot matrix printer.

(5*9 = 45 marks)