

QP CODE: 24900081



Reg No:.....

Name:.....

MAHATMA GANDHI UNIVERSITY, KOTTAYAM
FIRST SEMESTER MGU-UGP (HONOURS) REGULAR
EXAMINATION NOVEMBER 2024

First Semester

Discipline Specific Core Course - MG1DSCECT100, MG1DSCECC100 - EMERGING ELECTRONICS

(2024 ADMISSION ONWARDS)

Duration: 1.5 Hours

Maximum Marks: 50

Remember (K), Understand (U), Apply (A), Analyse (An), Evaluate (E), Create (C), Interest (I), Appreciation (Ap), and Skill (S)

Students should attempt atleast one question from each course outcome to enhance their overall outcome attainability.

[Learning Domain][CO No(s)]

Part A

Multiple Choice Questions

Answer all questions. Each question carries 1 mark

- 1 What is the relationship between the number of turns in the primary and secondary coils of a transformer and the voltage? [U] [1]
a) Directly proportional b) Inversely proportional
c) Unrelated d) Exponentially related
- 2 What is the unit of inductance? [U] [1]
a) Volt b) Ampere
c) Henry d) Ohm
- 3 Which of the following is a type of electronic system? [U] [1]
a) Power supply b) Amplifier
c) Filter d) All of the above
- 4 What type of wave does a half-wave rectifier produce? [U] [2]
a) Pure sine wave b) Full-wave rectified

- 16 How does a Miniature Circuit Breaker (MCB) protect against short circuits? [U] [3]

(4 × 5 = 20)

Part C

Essay Questions

Answer 2 questions. Each question carries 10 marks

- 17 Relate AC and DC signals to electronic devices, explaining their applications. [U] [1]
- 18 Describe how a transistor operates as an amplifier, including the importance of biasing and its applications in electronic devices. [U] [2]
- 19 Describe the working of a center-tapped full-wave rectifier, including the role of each component and its advantages over a half-wave rectifier. [A] [2]
- 20 What is an LDR? Describe the applications of Light Dependent Resistors (LDRs) in real-world devices and systems. [K] [3]

(2 × 10 = 20)

END OF THE QUESTION PAPER
